

than for other possible realizations, however. When realizing combinational circuits, for which the speed of operation is not crucial and which can be composed of identical cells, iterative networks prove to be very useful and economical.

## Notes and references

---

The finite-state model described in this chapter was proposed by Mealy [7] in 1955, on the basis of earlier models by Huffman [3] and Moore [8]. The applicability of the model to iterative combinational circuits was pointed out by McCluskey [6]. Recently, there have been several texts devoted to finite-state machines, among which are Hill and Peterson [2], Katz [4], Mano and Ciletti [5], and Wakerly [10]. A collection of original basic papers dealing with various aspects of finite automata is available in a book edited by Moore [9]. A comprehensive presentation of iterative networks is available in Hennie [1].

- [1] Hennie, F. C.: *Iterative Arrays of Logical Circuits*, MIT Press, Cambridge MA, 1961.
- [2] Hill, F. J., and G. R. Peterson: *Computer Aided Logical Design With Emphasis on VLSI*, fourth edition, John Wiley & Sons, New York, 1993.
- [3] Huffman, D. A.: "The synthesis of sequential switching circuits," *J. Franklin Inst.*, vol. 257, pp. 161–190, March 1954; pp. 275–303, April 1954. Reprinted in Moore [9].
- [4] Katz, R. H., and G. Borriello: *Contemporary Logic Design*, second edition, Pearson Prentice Hall, Upper Saddle River NJ, 2005.
- [5] Mano, M. M., and M. D. Ciletti: *Digital Design*, fourth edition, Prentice Hall, Upper Saddle River, NJ, 2007.
- [6] McCluskey, E. J.: "Iterative combinational switching networks: general design considerations," *IRE Trans. Electron. Computers*, vol. EC-7, pp. 285–291, December 1958.
- [7] Mealy, G. H.: "A method for synthesizing sequential circuits," *Bell System Tech. J.*, vol. 34, pp. 1045–1079, September 1955.
- [8] Moore, E. F.: Gedanken-experiments on sequential machines, pp. 129–153, *Automata Studies*, Princeton University Press, 1956.
- [9] Moore, E. F. (ed.): *Sequential Machines: Selected Papers*, Addison Wesley, Reading, Mass., 1964.
- [10] Wakerly, J. F.: *Digital Design Principles and Practices*, Prentice Hall, Englewood Cliffs NJ, 1990.

## Problems

---

**Problem 9.1.** Analyze the synchronous circuit of Fig. P9.1 (the clock is not shown, but is implicit).



- (d) The output  $z$  has the value 1 whenever the last four input symbols correspond to a BCD number that is a multiple of 3, i.e., 0, 3, 6, ...

**Problem 9.6.** Design a one-input one-output synchronous sequential circuit that produces an output symbol  $z = 1$  whenever any of the following input sequences occurs: 1100, 1010, or 1001. The circuit resets to its initial state after an output symbol 1 has been generated.

- (a) Form the state diagram or table. (Seven states are sufficient.)  
 (b) Choose an assignment, and show the excitation functions for  $JK$  flip-flops.

**Problem 9.7.** Design a one-input one-output synchronous sequential circuit that examines the input sequence in nonoverlapping strings having three input symbols each and produces an output symbol 1 that is coincident with the last input symbol of the string if and only if the string consisted of either two or three 1's. For example, if the input sequence is 010101110, the required output sequence is 000001001. Use  $SR$  flip-flops in your realization.

**Problem 9.8.** Design a modulo-8 counter that counts in the way specified in Table P9.8. Use  $JK$  flip-flops in your realization.

**Table P9.8**

Decimal	Gray code		
0	0	0	0
1	0	0	1
2	0	1	1
3	0	1	0
4	1	1	0
5	1	1	1
6	1	0	1
7	1	0	0

**Problem 9.9.** Construct the state diagram for a synchronous sequential machine that can be used to detect faults in coded messages of the 2-out-of-5 type. That is, the machine examines the messages serially and produces an output symbol 1 whenever an illegal message of five binary digits is detected.

**Problem 9.10.** When a certain serial binary communication channel is operating correctly, all blocks of 0's are of even length and all blocks of 1's are of odd length. Show the state diagram or table of a machine that will produce an output symbol  $z = 1$  whenever a discrepancy from the above pattern is detected. The following is an example.

$X : 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ \dots$   
 $Z : 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ \dots$


**Problem 9.11.** A new kind of flip-flop has been designed. It is equivalent to an  $SR$  flip-flop with gated inputs, as shown in Fig. P9.11.

A synchronous sequential circuit that generates an output symbol  $z = 1$  whenever the string 0101 is scanned in the input sequence is to be designed. Overlapping strings

are accepted; for example, corresponding to the input sequence 0010101, the required output sequence is 0000101.

- (a) Construct the state diagram and table for the circuit, using the letters  $A, B, C$ , etc.
- (b) Make a state assignment (use a Gray code, starting with an all-0 assignment for the initial state).
- (c) Realize the sequential circuit using the new flip-flops as memory elements. Give the logic equations for the memory elements and the output.

Fig. P9.11

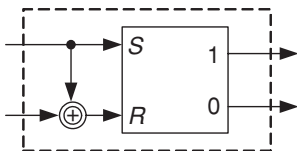

**Problem 9.12.** The clocked memory device shown in Fig. P9.12 has one binary input  $Y$  and one binary output  $y$ . If  $Y(t) = 0$  then  $y(t + 1) = 0$ ; if  $Y(t) = 1$  then  $y(t + 1) = y'(t)$ .

- (a) The state table given in Table P9.12 is to be realized using two such memory devices. Choose an appropriate state assignment and give the corresponding excitation and output equations.
- (b) Briefly discuss the possibility and practicality of using such memory devices to realize an arbitrary state table.

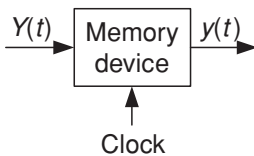


Fig. P9.12

Table P9.12

$PS$	$NS, z$	
	$x = 0$	$x = 1$
$A$	$B, 0$	$B, 0$
$B$	$C, 0$	$A, 1$
$C$	$B, 0$	$D, 0$
$D$	$C, 0$	$B, 1$

**Problem 9.13.** Write the state table for a synchronous circuit, with one input  $x$  and one output  $z$ , that operates according to the following specifications. At time  $t = 0$ , the initial state is  $A$ , and  $x(t) = 0$  for  $t < 0$ . The output function is given by either (a) or (b) as follows:

- (a)  $z(t) = x(t) + x(t - 1)$ ,
- (b)  $z(t) = x(t) \cdot x(t - 1)$

where the change from (a) to (b) occurs at times  $\tau$  such that

$$x(\tau) = x(\tau - 1) = x(\tau - 2) = 1$$

and the change from (b) to (a) occurs at times  $T$  such that

$$x(T) = x(T - 1) = x(T - 2) = 0.$$

An example is shown in Fig. P9.13.

Fig. P9.13

$t =$	0	1	2	3	4	5	6	7	8	9	10	11	12	...
$x(t) =$	0	1	1	1	0	0	1	1	0	0	0	1	0	...
$z(t) =$	0	1	1	1	0	0	0	1	0	0	0	1	1	...
	(a)				(b)						(a)			

**Problem 9.14.** The synchronous circuit shown in Fig. P9.14, where  $D$  denotes a unit delay, produces a periodic binary output sequence. Assume that initially  $x_1 = 1$ ,  $x_2 = 1$ ,  $x_3 = 0$ ,  $x_4 = 0$  and that the initial output sequence is 1100101000. Thereafter, this sequence repeats itself. Find a minimal expression for the combinational circuit  $f(x_1, x_2, x_3, x_4)$ .

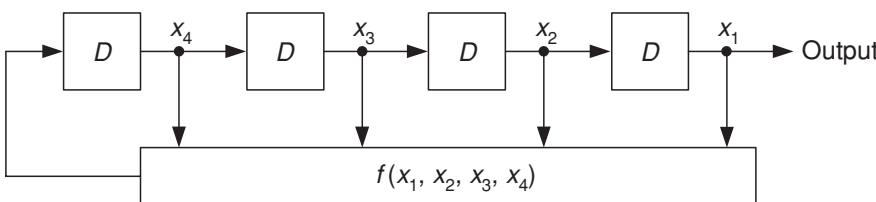


Fig. P9.14

**Problem 9.15.** A synchronous machine  $N$  is part of a transmitter and is used to encode binary serial messages. The coded messages are then transmitted to a receiver, as shown in Fig. P9.15. The receiver contains a synchronous machine  $M$  that is used to decode the received messages.

- (a) Given that the initial state of  $N$  is  $A$ , find the state diagram of machine  $M$ .
- (b) Suppose the initial state of  $N$  is unknown and machine  $M$  received a 10-bit message; which of the 10 bits can be uniquely decoded without an error? Explain.

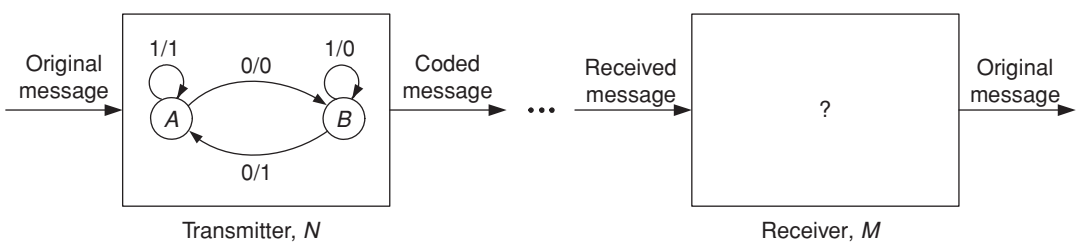


Fig. P9.15

**Problem 9.16.** A *palindrome* is a sequence which reads the same backward as forward, e.g., 11011 or 01010. Show the finite-state control of a Turing machine that is capable of detecting arbitrarily long palindromes. Assume that you are given a tape initially marked only with symbols #, 0, 1, where the blanks (#) separate blocks of intermixed 0's and 1's. The machine will be started on a # and then checks whether the sequence to its right is a palindrome. If not, the machine should proceed to the next block. If the sequence is a palindrome, the machine should stop at the # to the right of the block. An example is shown in Fig. P9.16.



**Problem 9.20.** The typical cell of an iterative network has one binary input  $x_i$  and one binary output  $z_i$ . The output  $z_i = 1$  if and only if  $x_i \neq x_{i-2}$ . For the first two cells (i.e.,  $i = 1, 2$ ), assume that  $x_{-1} = x_0 = 0$ .

- (a) Construct a cell table.
- (b) Make a Gray-code state assignment and give the output and carry functions.